 



**VDTT (JVL/JVY) Admissions, IIT Delhi**  
**Written screening, 2022**

1. An ADC has a sampling rate of 10 kHz. The frequency of the analog input is 8 kHz. What is the fundamental frequency observed at the output of the ADC?
  - A) DC
  - B) 2 kHz
  - C) 8 kHz
  - D) 12 kHz

2. In the circuit shown in the figure below, what is the 3-dB bandwidth of  $V_{out}/V_{in}$ ?




 - A)  $1/(RC)$
  - B)  $1/(2RC)$
  - C)  $\infty$
  - D)  $2/(RC)$
3. In the circuit shown in the figure below, the nMOS device has  $V_{TH}$  of 0.2 V,  $\mu_n C'_{ox} W/L$  of  $200 \mu\text{A}/\text{V}^2$ . What is the current in the nMOS device?




- A) 0.0554 mA
  - B) 1 mA
  - C) 0.707 mA
  - D) 1 mA

 
4. In the circuit below, what is  $V_{out}/V_{in}$ ?



 - A)  $-R_3/(R_1 + R_2)$   
 B)  $-R_3/R_1$   
 C)  $R_3/(R_1 \parallel R_2)$   
 D)  $-(R_3 \parallel R_2)/R_1$
5. In the circuit below,  $\omega$  is the resonant frequency of the RLC circuit. The highest value of  $v_o(t)$  is:




 - A) 1 mV  
 B) 100 mV  
 C) 10 V  
 D) 1 kV
6. What is the small signal gain,  $v_o/v_{in}$ , of the circuit shown in the figure below?




- A) -2
- B) 2
- C) 0
- D)  $\infty$

 7. The circuit shown in the figure below is a/an:



- A) AND gate
- B) NAND gate
- C) OR gate
- D) NOR gate

 
8. The voltage gain,  $V_{out}/V_{in}$ , of the circuit in the figure below is approximately 1. Which of the following statements is true?




- A) A, C are negative; B, D are positive.
- B) A, D are negative; B, C are positive.
- C) B, C are negative; A, D are positive.
- D) B, D are negative; A, C are positive.

9. Which of the following statements is true about the circuit shown in the figure below?  $Z_{in}$  represents the impedance of the circuit while

looking in the direction of the arrow.

 

 - A)  $Z_{in} = sC/g_m^2$  and the impedance behaves like an inductor.
  - B)  $Z_{in} = g_m^2/sC$  and the impedance behaves like a capacitor.
  - C)  $Z_{in} = g_m^2/C$  and the impedance behaves like a resistor.
  - D)  $Z_{in} = g_m/sC$  and the impedance behaves like a capacitor.
10. In the circuit shown below the transconductances of the nMOS and pMOS devices are the same. The output resistance of the nMOS and pMOS devices are the same.  $g_{mb}$  is 0. The differential voltage gain,  $(v_{out}^+ - v_{out}^-)/(v_{in}^+ - v_{in}^-)$  is:



- A) -1
  - B) 1
  - C) -1/2
  - D) 2
11. A Miller compensated OTA with a unity gain bandwidth of 20 MHz has a  $g_m$  of 250  $\mu S$  in its first stage. The compensation capacitor used is approximately:

- A) 1 pF

- B) 2 pF  
C) 3 pF  
D) 5 pF
12. The source of a MOS device biased in saturation is terminated with a resistance  $R$ . The small signal incremental impedance looking into the drain of the circuit is:
- A)  $R + r_{ds} + g_m r_{ds}$   
B)  $\frac{r_{ds} + R}{1 + g_m r_{ds}}$   
C)  $1/g_m$   
D)  $R + 1/g_m$
13. In a 2-stage cascode current mirror designed with pMOS devices, the maximum voltage tolerable at the output of the circuit, such that the circuit works as a current source, is:
- A)  $V_{DD} - 2V_{GST}$   
B)  $V_{DD} - V_{GST} - V_T$   
C)  $V_{DD} - 2V_{GST} - 2V_T$   
D)  $V_{DD} - 2V_{GST} - V_T$
14. An n-channel MOS device is biased at the edge of saturation (i.e., pinch-off.) The  $C_{gd}$  of the device is:
- A)  $2C_{ox}/3$   
B)  $C_{ox}/2$   
C)  $C_{ox}/3$   
D)  $C_{ox}/4$
15. Evaluate the following integral in a counter-clockwise loop given by  $|z - 1| = 1$ .

$$\oint \frac{2z}{z^2 - 1} dz$$

- A)  $4\pi j$   
B)  $2\pi j$   
C) 0  
D)  $-2\pi j$

16. The setup time of a flip-flop is 10 ps, the hold-time is 50 ps, the delay of the flip-flop is 10 ps. The delay of logic circuits in feedback is 70 ps. What is the maximum frequency of the clock that can be used to operate the state-machine correctly?
- A) 7.1 GHz
  - B) 7.7 GHz
  - C) 11.1 GHz
  - D) 14.2 GHz
17. A traffic light signal has a three-digit BCD seconds counter that can count down from 120 to 0 seconds. What is the minimum number of flip-flops that are required to operate this counter?
- A) 12
  - B) 9
  - C) 8
  - D) 7
18. What is the asymptotic time complexity of the merge-sort algorithm?
- A)  $O(N)$
  - B)  $O(N \log N)$
  - C)  $O(N^2)$
  - D)  $O(1)$
19. What is the best (fastest) way of finding the third-largest number in an unsorted array?
- A) Sort the array and then find the number that is the third from the top.
  - B) Make a single pass on the array and use a small decision tree.
  - C) Make two passes on the array.
  - D) Make three passes on the array.
20. What is the advantage of the 2's complement notation?
- A) It has a single representation for 0.
  - B) Multiplying two signed numbers is equivalent to multiplying their unsigned representations (in a 2's complement form).

- C) Subtraction is easy.
- D) All the options.